 


Columbus Joint Chapter
SSC37 / CAS04

Presentation will
begin at 6:15 EST





SSC37/CAS04



Columbus Joint-Chapter Seminar

A Practical Approach to Lab-to-Fab series: Tiny Tapeout Workshop (2)


Webinar Location: SenselCs Corporation @ Rev1 Ventures Main
Conference Room
Speaker: Sam Ellicott

About Me

 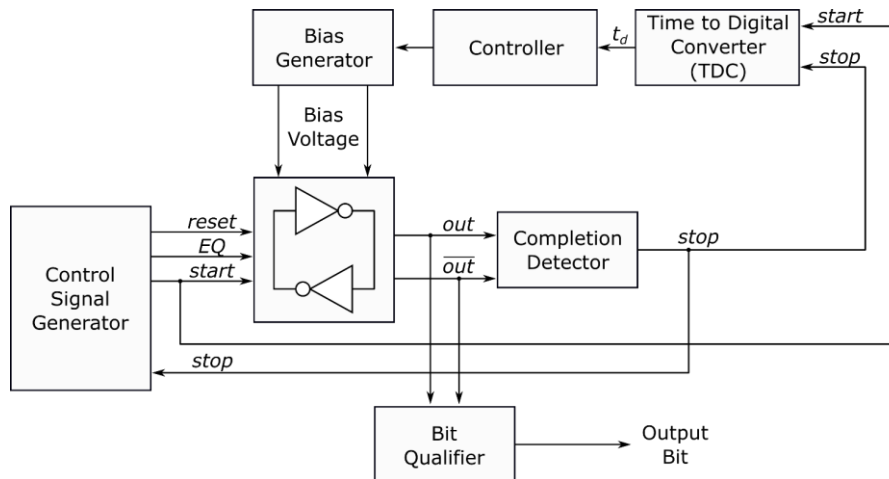- IEEE Columbus SSCS/CAS Webmaster
- PhD Student at The Ohio State University
 - Circuits Laboratory for Advanced Sensors and Systems
 - RF and Mixed-Signal Integrated Circuit (IC) Design
 - True Random Number Generators
- BSEE at Cedarville University (2019)
- Intern at Analog Devices




Workshop Series Goals

 


- Understand the workflow for open-source tools
 - Demystify the steps required to generate digital designs
- Hands-on introduction to digital design
 - Crash course to Verilog
 - Ability to design/test simple modules
 - Make a simple project
- Have fun!

Workshop Series Outline

 


- Workshop 1: Introduction
 - Last Semester
- Workshop 2: Tooling and Series Project
 - Today
- ~~• Workshop 3: Design Review~~
 - ~~• October/November~~

Workshop Series Outline

 

- Workshop 1: Introduction
 - What are Integrated Circuits (ICs)
 - Brief History of ICs
 - Introduction to Digital Design
 - Introduction to Tiny Tapeout
- Workshop 2: Tooling and Series Project

Workshop Series Outline

 


- Workshop 1: Introduction
- Workshop 2: Tooling and Series Project (tonight)
 - Review of Workshop 1
 - Set up a Tiny Tapeout project
 - Write simple Verilog modules
 - Write simple Verilog testbenches




Background/Review

What are we trying to do?

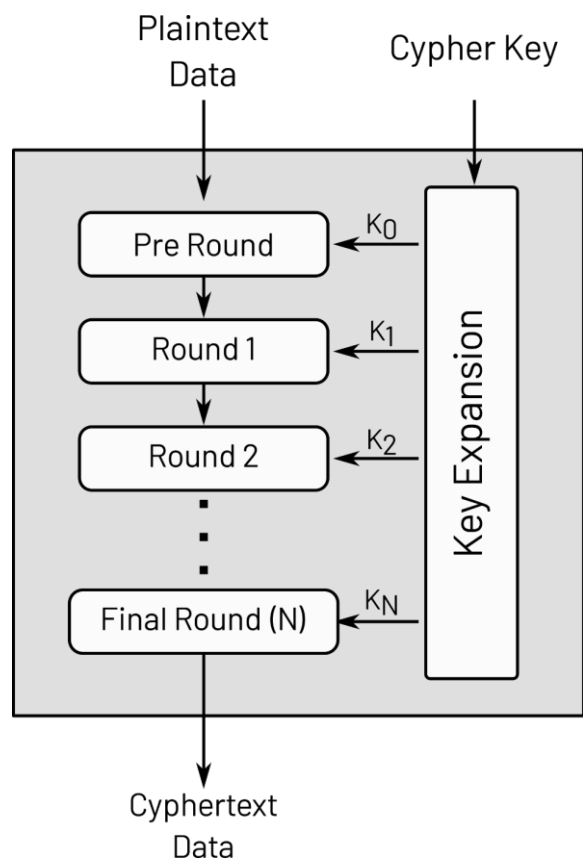- Concept (algorithm, behavior, etc) → Physical design (gates)



Digital Design Flow
(OpenLane)

 

Recap: Digital Design

- Concept (algorithm, behavior, etc) → Physical design (gates)

```

reg [WIDTH-1:0] iteration;
reg [WIDTH-1:0] prev;
reg [WIDTH-1:0] current;

assign o_busy = (iteration != RESET);
assign o_fib = current;



always @(posedge i_clk) begin
  if (i_reset || (!o_busy && i_stb)) begin
    iteration <= i_n;
    prev [WIDTH-1:0] <= 1;
    current [WIDTH-1:0] <= 0;
  end
  else if (o_busy) begin
    iteration <= iteration - ONE;
    current <= prev + current;
    prev <= current;
  end
end

if (i_reset) begin
  iteration <= RESET;
  prev [WIDTH-1:0] <= 1;
  current [WIDTH-1:0] <= 0;
end

endmodule

```

NORMAL fib.v

 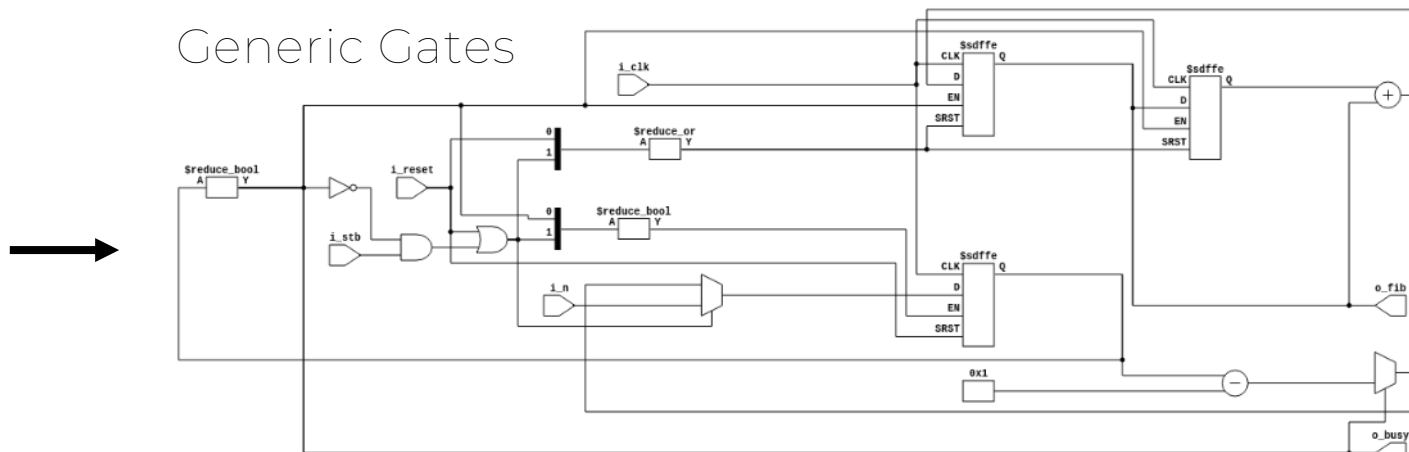


OpenLane Flow


WOKwi

or

Verilog Files

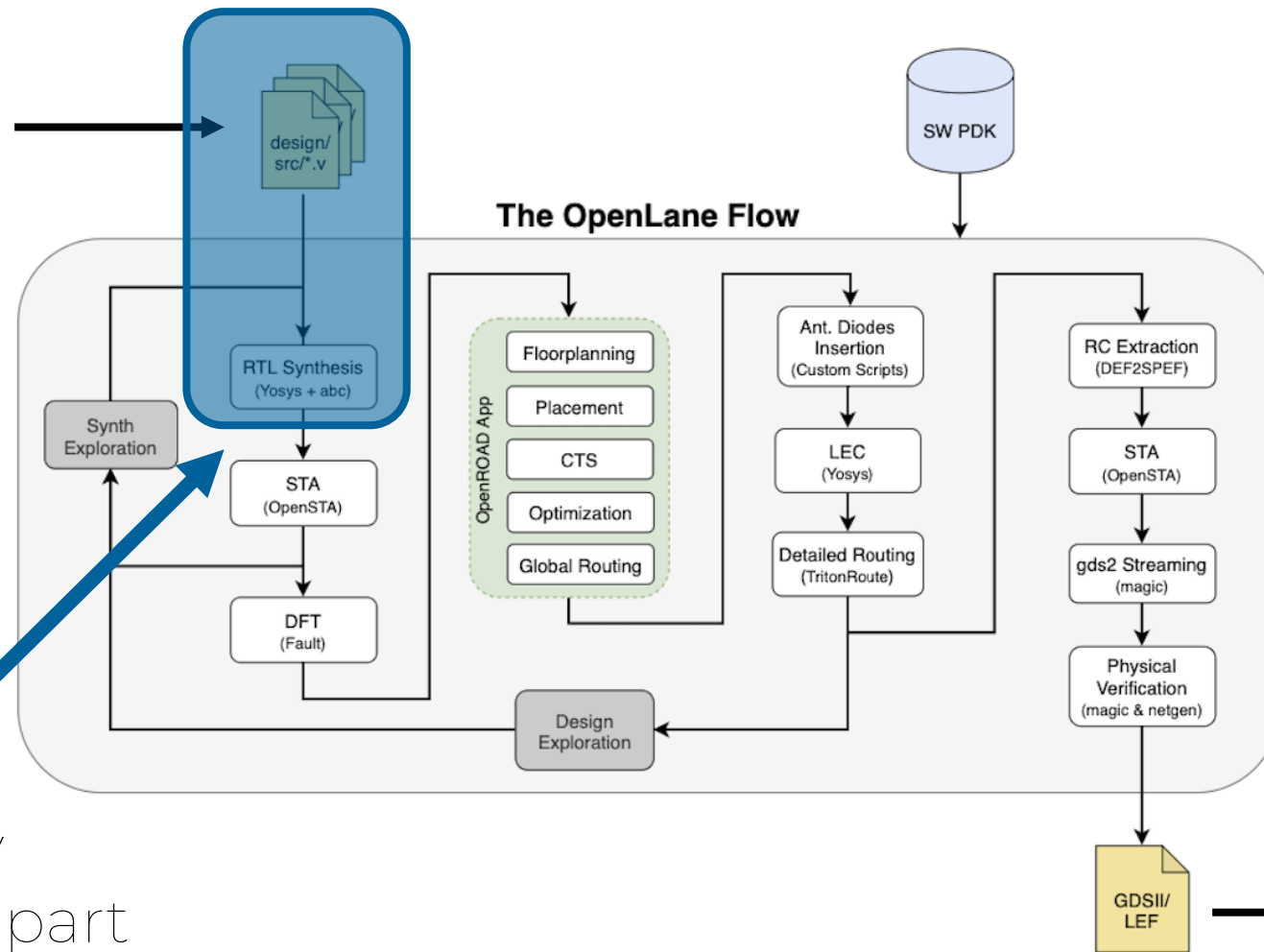

Output Design (GDS File)

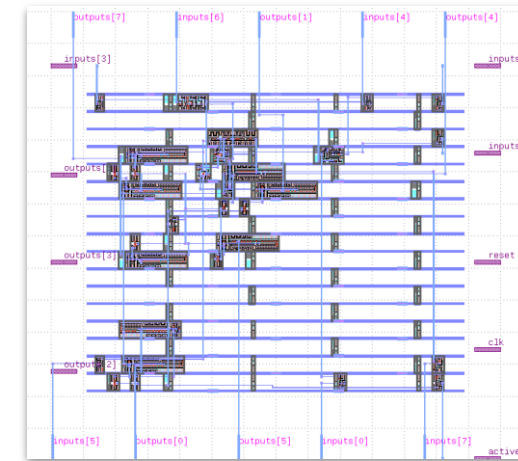


We're mostly dealing with this part

Tiny Tapeout (via Openlane) handles most of this for us!



How Tiny Tapeout Works

 - Cloud based design
 - Runs OpenLane in Github actions
 - No tool install or download
 - 3D viewer / explorer
 - [Example Design](#)
- ~500 Projects merged into one IC
 - Reduced cost
 - Try other peoples designs
 - [Test PCB](#)





How

 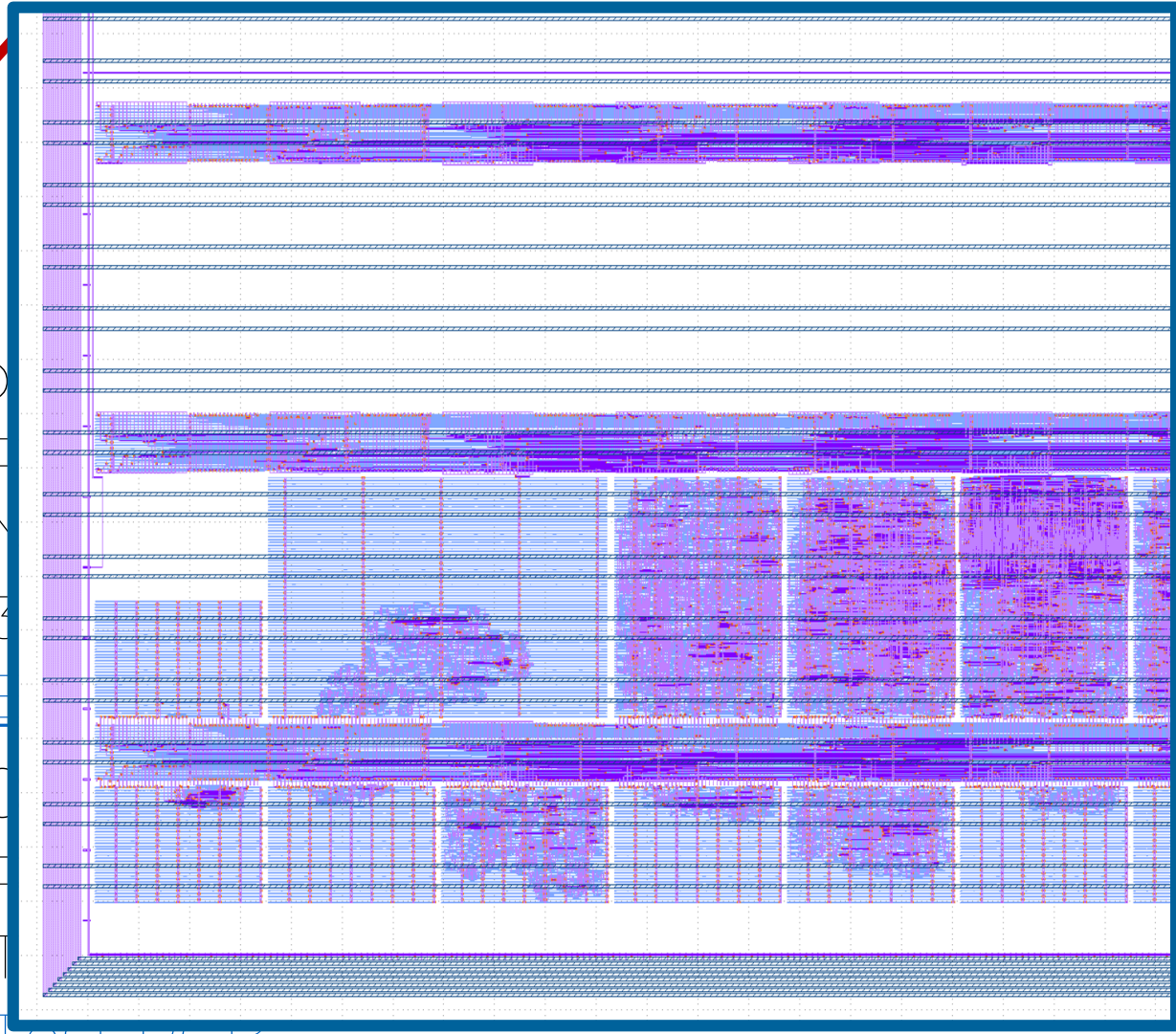
- Clock
- Power
- Memory
- CPU
- Ethernet
- ~50
- F
- T
- Test PCB



Physical Interface

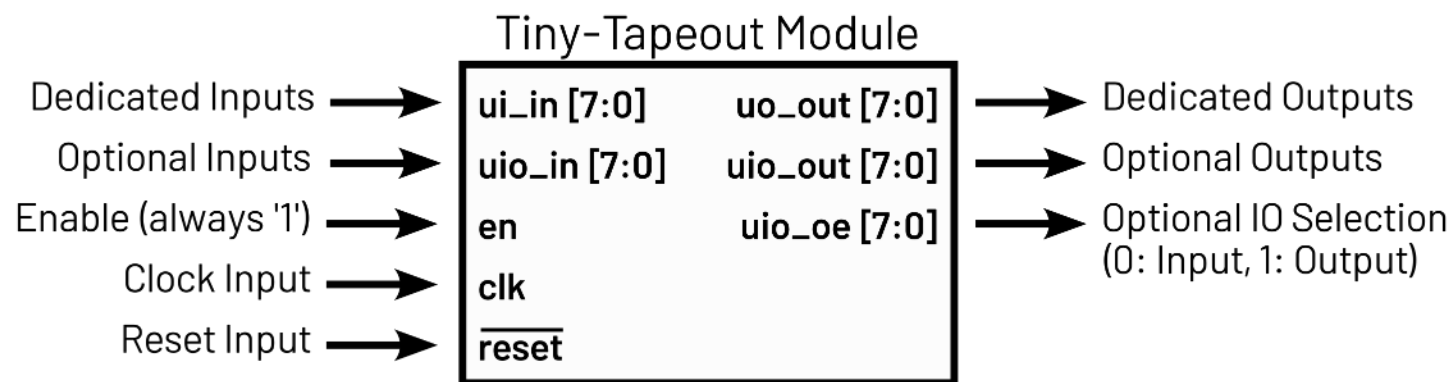 
- 1x Tile
 - 160 x 100 μm size
 - ~1000 gates
 - Can buy more than 1 tile
- Pins
 - Clock (~50MHz)
 - Reset
 - 8x Inputs
 - 8x Outputs
 - 8x Bidirectional



 


Workshop Project

Project Introduction

 

- Design a 7-Segment Digital Desk Clock
 - 24 Hour time format
 - Time set
 - 7-Segment Display Output
 - Easily extensible for customization
- Broken into modules
 - Some provided
 - Some are yours to complete 😊
- Testbenches for each module


Desk Clock Block Diagram Overview

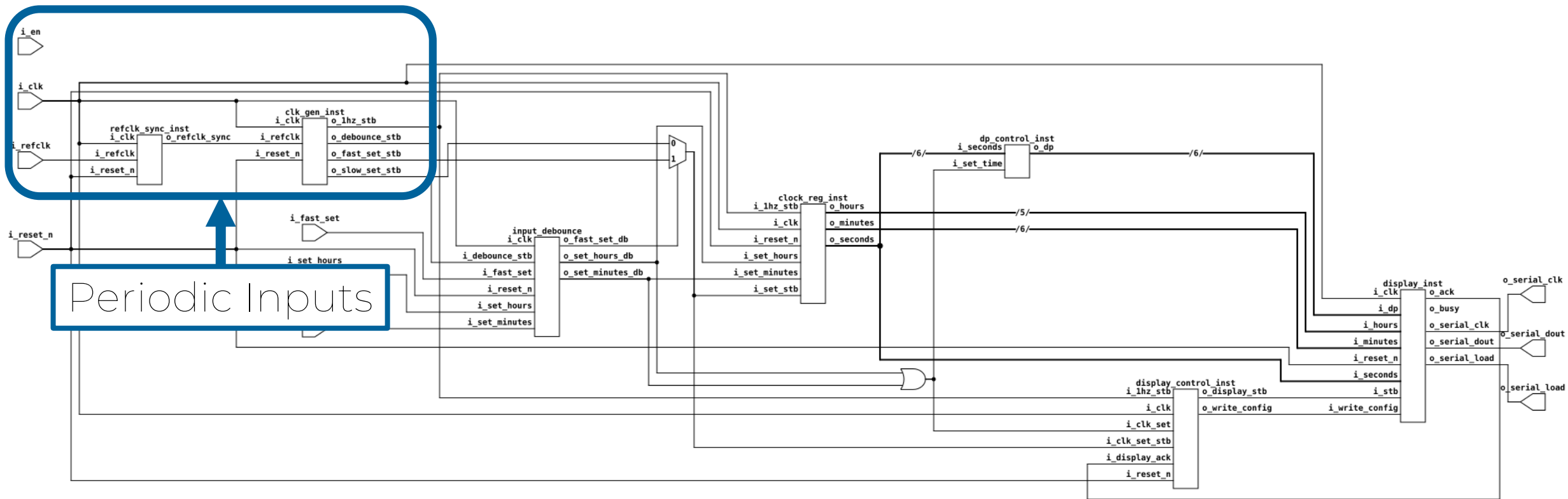

Periodic Inputs


- Generate “strobe” signals to trigger update events
 - Strobe signal is a single system clock wide pulse

Desk Clock Block Diagram Overview

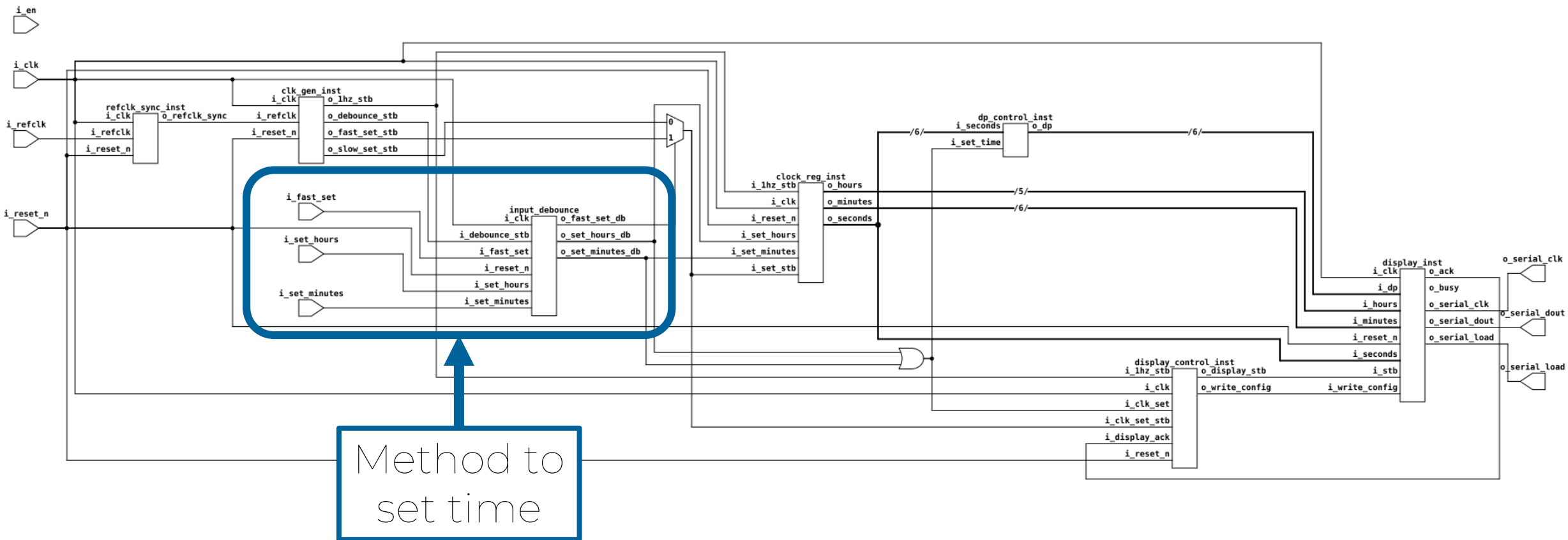


- Synchronize and Debounce Button Inputs
 - Clean up noisy signals

Desk Clock Block Diagram Overview

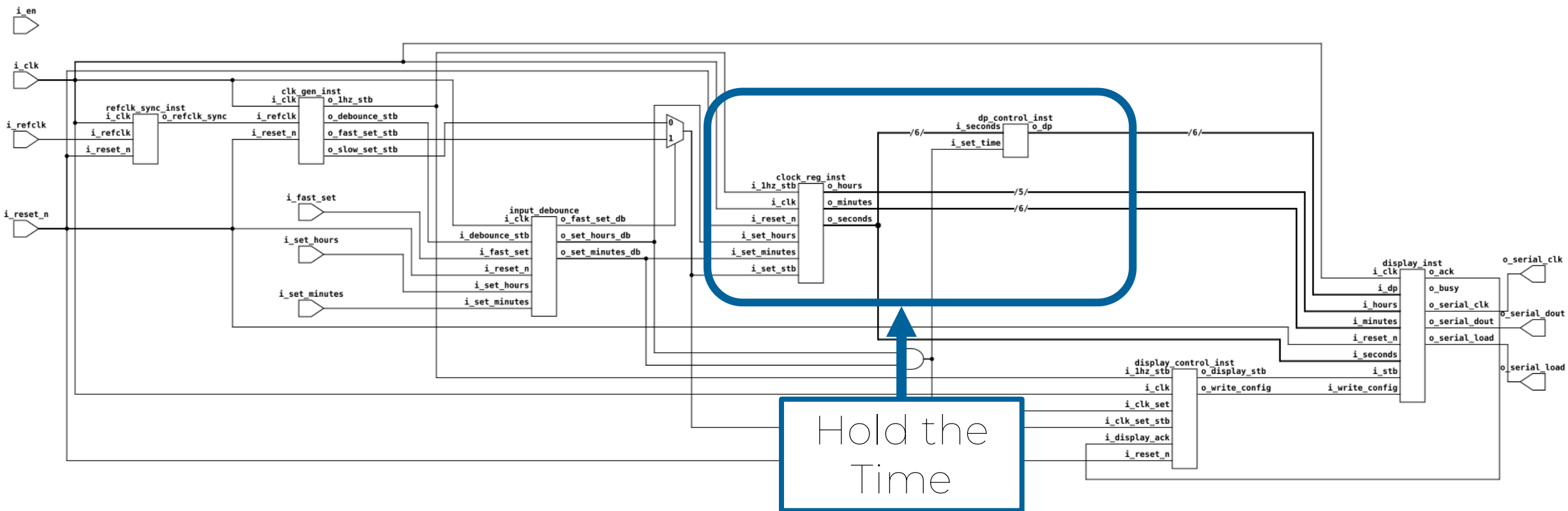

- Hold the time in 24-Hour format
- Wrap Hours, Minutes, Second appropriately
- Handle time setting functionality


Desk Clock Block Diagram Overview

 

- Shift out time over SPI
 - Drive MAX7219 Display


<https://www.diymore.cc/products/max7219-7-segment-led-dot-matrix-8-digit-digital-tube-display-control-module-for-arduino-3-3v-5v-microcontroller-serial-driver>

Desk Clock Block Diagram

 


- Everything runs off a single system clock
- Reference clock provides accurate timing ($2^{15} Hz$)

Desk Clock Block Diagram

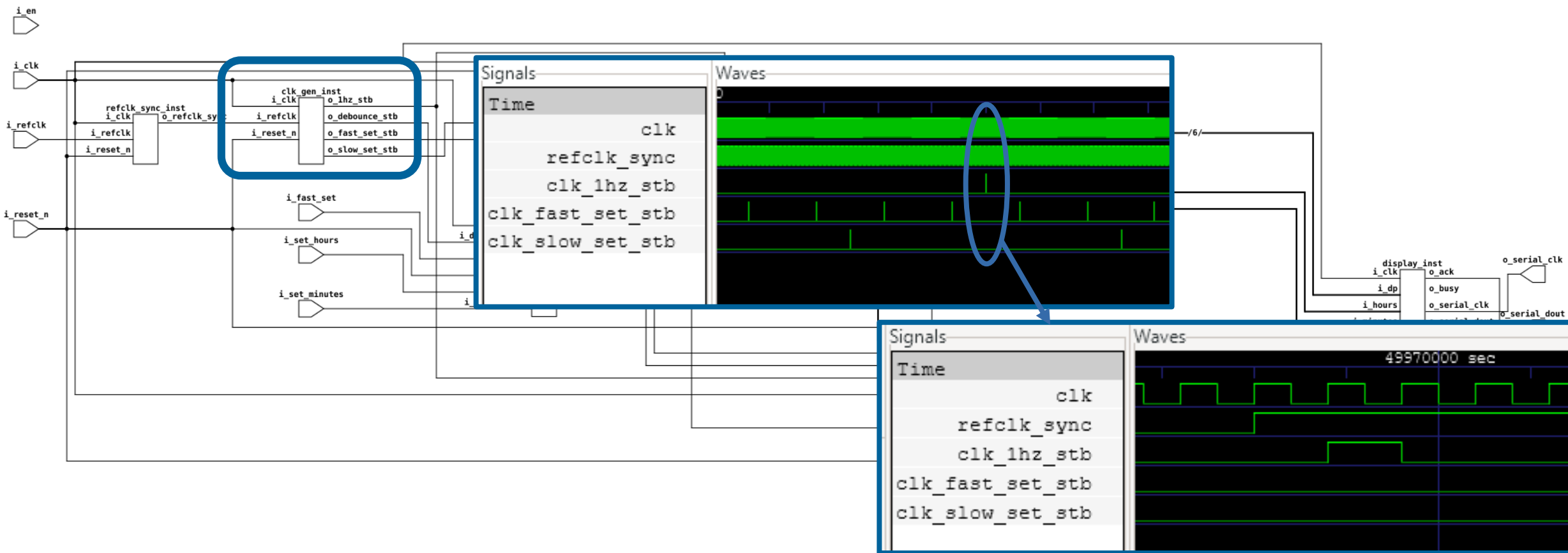


- Generate “strobe” signals to trigger update events
 - Strobe signal is a single system-clock wide pulse

Desk Clock Block Diagram

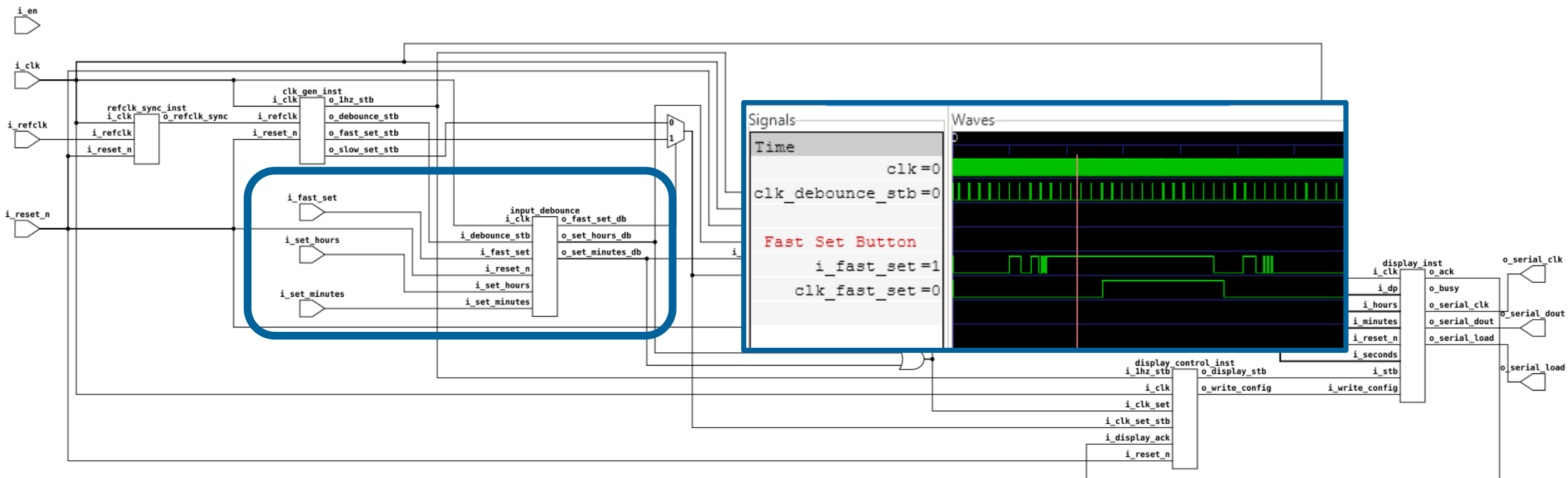


- Synchronize and Debounce Button Inputs
 - Clean up noisy signals

Desk Clock Block Diagram Overview

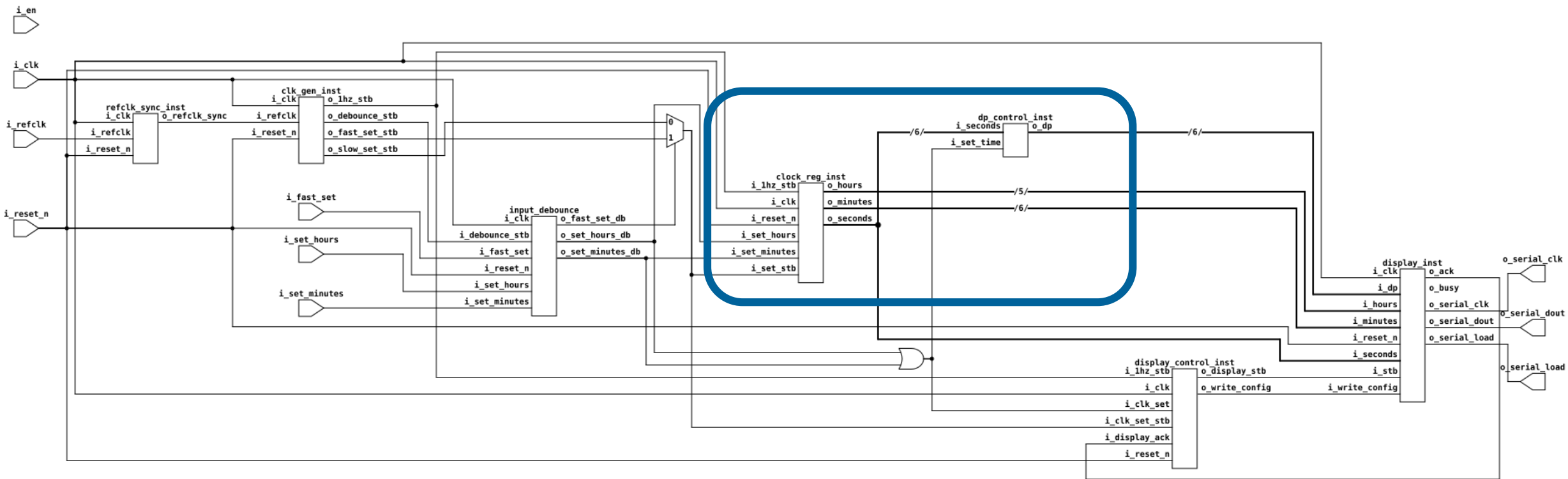

- Hold the time in 24-Hour format
- Wrap Hours, Minutes, Second appropriately
- Handle time setting functionality


Desk Clock Block Diagram

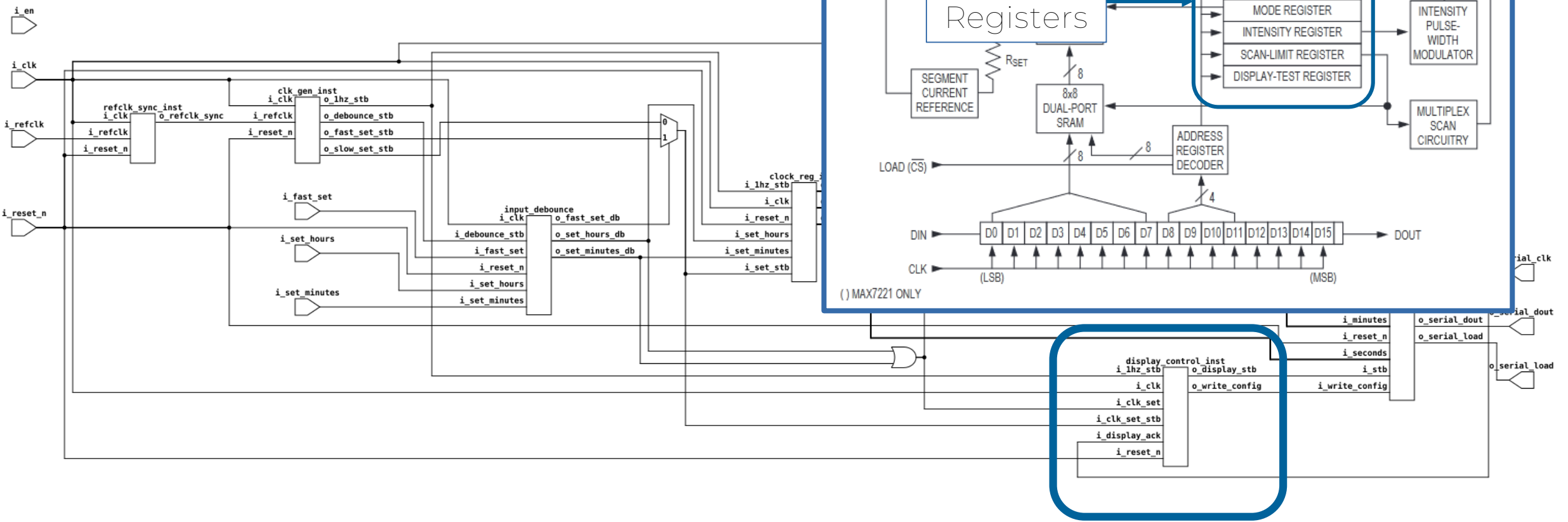

- MAX7219 Needs Configured
 - Write display settings on startup


<https://www.analog.com/media/en/technical-documentation/data-sheets/MAX7219-MAX7221.pdf>

What are we doing?

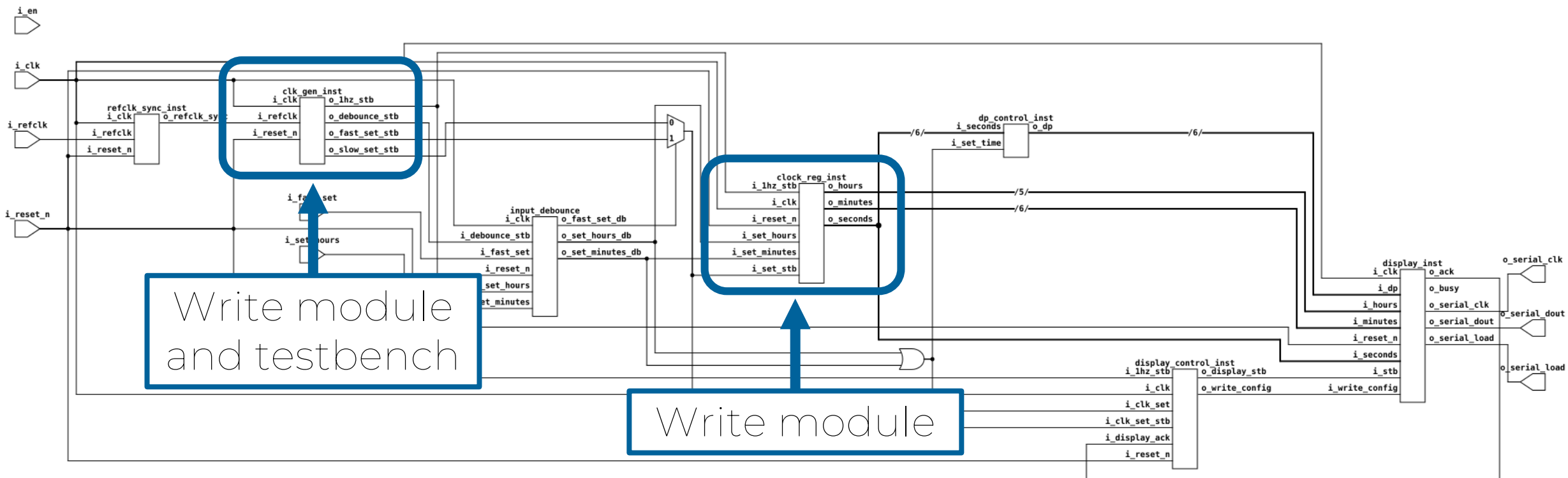


- Implement a few blocks
 - Strobe signal generator
 - Clock register

Where do we go from here?

 


1. Tools/Project Setup
2. Write “Strobe Generation” Module
 - Verilog Crash Course
 - Generating Block Diagrams
3. Write “Strobe Generation” Testbench
 - View results in gtkwave
4. Repeat for “Clock Register” (If we have time)
 - Testbench is already done for this module
5. Run Tiny Tapeout flow to generate hardware

Start a Project (1/2)

 


The screenshot shows a GitHub repository page for 'sellicott / sellicott_tt_7seg_clock_2024'. The repository is a public template generated from 'TinyTapeout/tt09-verilog-template'. The page includes navigation tabs for Code, Issues, Pull requests, Actions, Projects, Security, Insights, and Settings. A dropdown menu is open from the 'Use this template' button, showing options: 'Create a new repository' and 'Open in Codespace'. A blue box with the text 'Make a new repo' has an arrow pointing to the 'Create a new repository' option. A blue box at the bottom of the page contains the URL: https://github.com/sellicott/sellicott_tt_7seg_clock_2024. The repository's commit history is visible, showing a commit by Samuel Ellicott titled 'Fix typo in readme' and several folders like '.devcontainer', '.github/workflows', and '.vscode'.

Start a Project (2/2)

 


The screenshot shows the GitHub interface for the repository 'sellicott/sscs-cass_desk_clock_project'. A 'Code' button is highlighted in green, with a callout box 'Download repo to USB Drive' pointing to it. A dropdown menu is open, showing options: 'Clone' (with sub-options for HTTPS, SSH, and GitHub CLI), 'Open with GitHub Desktop', and 'Download ZIP'. A callout box 'Download Code' points to the 'Code' button. Another callout box 'Copy URL' points to the SSH URL 'git@github.com:sellicott/sscs-cass_desk_cloc'. A third callout box 'Download Zip' points to the 'Download ZIP' option. The repository file list includes folders like '.devcontainer', '.github/workflows', '.vscode', 'docs', 'src', 'test', and files like '.gitignore'. The repository is marked as 'Public' and 'generated from sellicott/sellicott_tt_7seg_clock_2024'.

Start up tools

 

The screenshot shows a Windows File Explorer window titled 'sellicott_tt_7seg_clock_2024' with the address bar showing 'ESL-DNC193934D > USB Drive (D:) > sellicott_tt_7seg_clock_2024'. The file list includes folders like .vscode, docs, sim, src, test and files like .gitignore, elaborate_json.bat, info.yaml, LICENSE, netlistsvg.bat, README.md, start.bat, and clk_gen_tb.fst. The 'start.bat' file is selected and highlighted in red. A red circle with the number '1' and a red arrow points to it, with a callout box containing the text 'Double Click'. In the foreground, a terminal window is open with the command prompt 'D:\sellicott_tt_7seg_clock_2024>'. To the right, a blue-bordered callout box contains the text 'Startup Two Terminals' followed by a bulleted list: '• One for simulation' and '• One for gtkwave'.

Clone the repo

 

The screenshot shows a Windows File Explorer window displaying the contents of a USB drive (D:) named 'PortableGit'. The files listed are:

| Name | Date modified | Type | Size |
|-----------------|--------------------|---------------|--------|
| bin | 10/22/2024 6:33 AM | File folder | |
| cmd | 10/29/2024 4:03 AM | File folder | |
| dev | 10/22/2024 6:33 AM | File folder | |
| etc | 10/22/2024 6:33 AM | File folder | |
| mingw64 | 10/22/2024 6:33 AM | File folder | |
| tmp | 10/22/2024 6:33 AM | File folder | |
| usr | 10/22/2024 6:32 AM | File folder | |
| git-bash.exe | 10/22/2024 6:19 AM | Application | 136 KB |
| git-cmd.exe | 10/22/2024 6:19 AM | Application | 136 KB |
| LICENSE.txt | 10/22/2024 6:33 AM | Text Document | 19 KB |
| README.portable | 10/22/2024 6:33 AM | TABLE File | 4 KB |

Four numbered callouts indicate the steps:


- 1 Double Click**: Points to the `git-cmd.exe` file.
- 2 Type "cd /d"**: Points to the command prompt window where the user has entered `D:\PortableGit>cd /d U:\`.
- 3 Drag & Drop**: Points to the `git-cmd.exe` file in the File Explorer and the command prompt window.
- 4 Clone Repo**: Points to the command prompt window where the user has entered `U:\>git clone git@github.com:sellicott/sellicott_tt_7seg_clock_2024.git`.

<https://docs.github.com/en/authentication/keeping-your-account-and-data-secure/managing-your-personal-access-tokens>


Modify Project

- Look at github project page
 - Look at log messages to see why builds are failing
 - Setup github pages
- Move template files to their base names
 - Move ``src\input\clk_gen_template.v`` to ``src\input\clk_gen.v``
 - Move ``src\core\clock_register_template.v`` to ``src\core\clock_register.v``

Strobe Generation Module

 

Writing a Verilog Module

 

- We are going to write the strobe generation module
- Generate 1-clock wide pulses to trigger updates
 - Allow everything to run off the system clock
 - Rest of the system uses these strobe pulses
- Goals for this section
 - Learn to write a Verilog module
 - Learn how to generate block diagrams
 - Learn how to run Icarus verilog

Writing a Verilog Module

- Open ``src\input\clk_gen.v``
- We have a defined set of IO Pins
 - We want to generate strobe signals
 - Base the strobe signals off the refclk
- How do we do this?
 - Before we write code, what should the hardware look like?

```

`default_nettype none

module clk_gen (
  // global signals
  i_reset_n,
  i_clk,
  // Strobe from 32,768 Hz reference clock
  i_refclk,
  // output strobe signals
  o_1hz_stb, // refclk / 2^15 -> 1Hz
  o_slow_set_stb, // refclk / 2^14 -> 2Hz
  o_fast_set_stb, // refclk / 2^12 -> 8Hz
  o_debounce_stb // refclk / 2^4 -> 4.096KHz
);

input wire i_reset_n;
input wire i_clk;
input wire i_refclk;

output wire o_1hz_stb;
output wire o_slow_set_stb;
output wire o_fast_set_stb;
output wire o_debounce_stb;


// TODO: Implement strobe output signals

endmodule


```

The Completed Block (diagram)

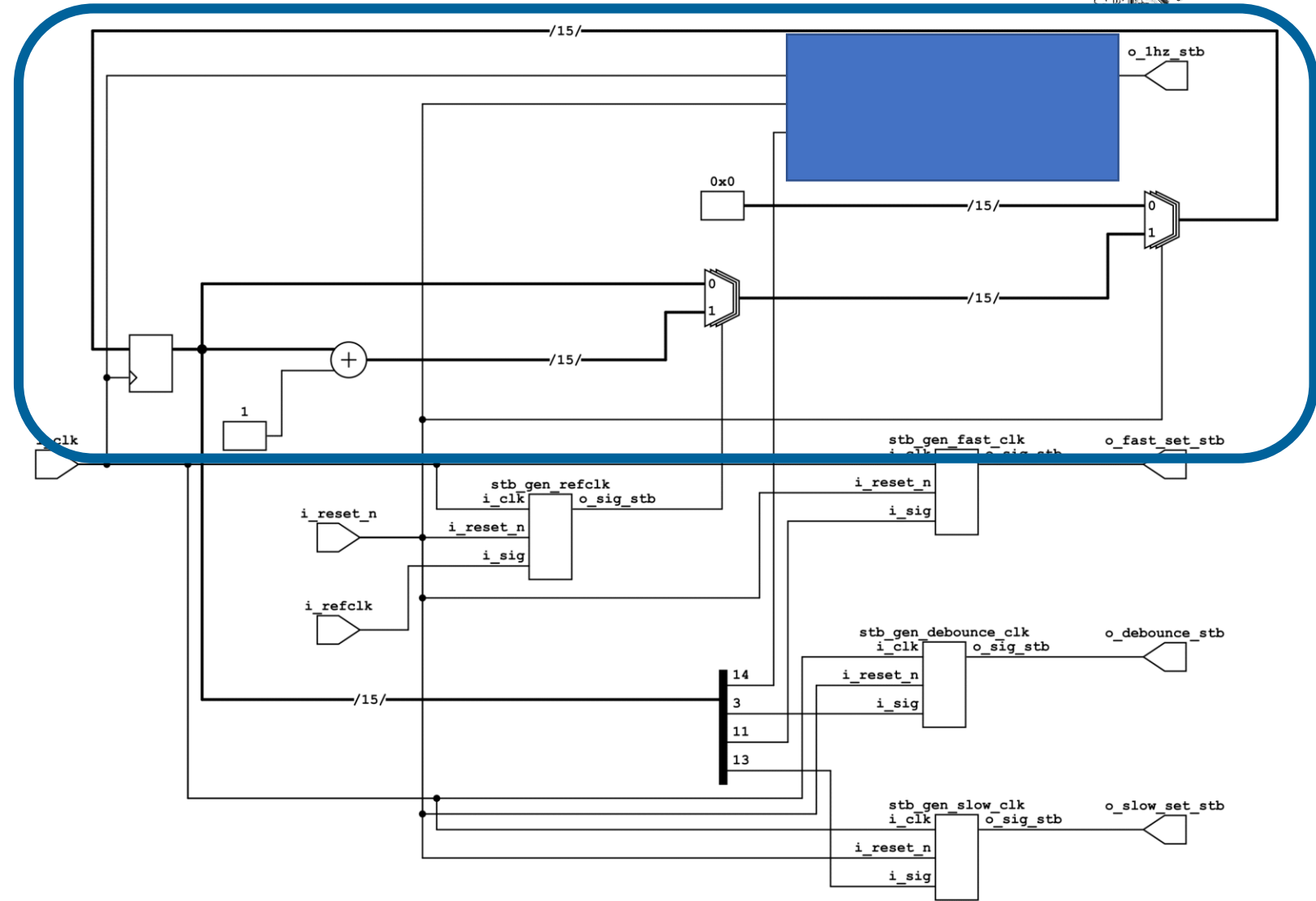- Looks daunting
- Break it down
 - Counter
 - Strobe generators
- How do we write a counter?




Crash course in Verilog

 

- For more detailed tutorials

- [NandLand](#)
- [ChipVerify](#)
- [ZipCPU](#)
- [Verilog Reference Card \(pdf\)](#)
- [Verilog Reference Manual \(pdf\)](#)
- [Verilog RTL Synthesis Standard \(pdf\)](#)

What gets turned into hardware?

 

- For now you have me...

- This will only cover the bare necessities for today's project
- I hope to motivate you to learn more

Verilog Basics

- What are we going to talk about
 - Modules
 - Sequential Logic (Flip-Flops)
 - Combinational Logic
- Preliminaries
 - Sort of “C like” syntax (if you squint)
 - Statements end with “;”
 - Case-sensitive names
 - Comments with “//” and “/* stuff */”
 - Blocks start/stop with **begin** and **end**
 - Give blocks a name using
 - **begin: block_name**

7.1. UNARY OPERATORS

| | |
|-----------|--------------------|
| +, - | Positive, Negative |
| ! | Logical negation |
| ~ | Bitwise negation |
| &, ~& | Bitwise and, nand |
| , ~ | Bitwise or, nor |
| ^, ~^, ^~ | Bitwise xor, xnor |

7.2. BINARY OPERATORS

Increasing precedence:

| | |
|------------------|--------------------------|
| ?: | if/else |
| | Logical or |
| && | Logical and |
| | Bitwise or |
| ^, ^~ | Bitwise xor, xnor |
| & | Bitwise and |
| ==, !=, ===, !== | Equality |
| <, <=, >, >= | Inequality |
| <<, >> | Logical shift |
| +, - | Addition, Substraction |
| *, /, % | Multiply, Divide, Modulo |

From: <https://www.ece.lsu.edu/v/refcard.pdf>

Lets write a counter!

- Edit “**src\input\clk_gen.v**”
- Divide our input **refclk** signal by 2^{15}
 - Generate **1Hz** clock signal
- We also need $\frac{\text{refclk}}{2^{14}}$, $\frac{\text{refclk}}{2^{12}}$, and $\frac{\text{refclk}}{2^4}$
 - Generates **2Hz**, **8Hz**, and **4.096KHz** clocks respectively
 - Tap off output clocks from the counter
- We need a 15-bit register
 - Reset to 0 with reset signal
 - Count up by 1 on each rising edge of **refclk**
 - We will come back to this...
 - For now, count up on **i_clk** rising edge



Verilog Modules

```

`default_nettype none

module clk_gen (
  // global signals
  i_reset_n,
  i_clk,
  // Strobe from 32,768 Hz reference clock
  i_refclk,
  // output strobe signals
  o_1hz_stb, // refclk / 2^15 -> 1Hz
  o_slow_set_stb, // refclk / 2^14 -> 2Hz
  o_fast_set_stb, // refclk / 2^12 -> 8Hz
  o_debounce_stb // refclk / 2^4 -> 4.096KHz
);

input wire i_reset_n;
input wire i_clk;
input wire i_refclk;

output wire o_1hz_stb;
output wire o_slow_set_stb;
output wire o_fast_set_stb;
output wire o_debounce_stb;

// TODO: Implement strobe output signals

endmodule

```



- Start files with this



- Module Port List
- List of names separated by commas
- By (my) convention
 - Inputs are **i_<name>**
 - Outputs are **o_<name>**



- Define Signal Wires/Registers
- Signals in the port list are prefixed with
 - **input** or **output**
- We can assign to wires when we create them
- We can define busses too
 - **wire [msb:lsb] bus_name;**

- In general:


```

module module_name ( list_of_signals );
// stuff
endmodule

```


Multi-Bit Signals

- Busses (groups of signals)
 - `wire [msb:lsb] bus_name;`
 - `reg [msb:lsb] bus_name;`
- Accessing Busses
 - `bus_name[bit]`
 - `bus_name[msb:lsb]`
 - `bus_name[bit1, bit2, msb:lsb]`
- Grouping Signals
 - `wire [2:0] signal_group = {sig_2, sig_1, sig_0};`
- Fixed Width Constants
 - Format: `<width>'<format><value>`
 - `<width>` is a decimal number > 0
 - `<format>` is a letter
 - `b` for binary
 - `o` for octal
 - `d` for decimal
 - `h` for hexadecimal
 - `<value>` is a number (in the appropriate format) that fits the width of the constant
 - Numbers can be separated by “_”
- Examples
 - `16'h5a5a_a5a5`
 - `5'd3`
 - `3b110`

Sequential Logic: Always @(posedge)

```
input wire i_reset_n;
input wire i_clk;
input wire i_refclk;

output wire o_1hz_stb;
output wire o_slow_set_stb;
output wire o_fast_set_stb;
output wire o_debounce_stb;

wire refclk_stb;
reg [14:0] refclk_div;
```

Define Signals

```
always @(posedge i_clk) begin
    if (refclk_stb) begin
        refclk_div <= refclk_div + 1;
    end
    if (!i_reset_n) begin
        refclk_div <= 15'h0;
    end
end
```

Sequential Logic Behavior

Low Priority

High Priority

- Always use system clock!
- Block “fires” on **i_clk** rising edge
- Note the **@(posedge signal)**
- start/stop with **begin/end**
- If / else if / else statements
 - Only in always blocks
 - start/stop with **begin/end**
- Assignment uses **<=**
 - Only assign to **reg** signals
 - Can read from regs and wires

Counter (as of right now)

- What do we expect?
- Block Diagram
 - 15-bit Flip-Flop
 - Triggered on **i_clk**
 - Add '1' when **i_reset_n** is high
 - Set to '0' when **i_reset_n** is low
 - Assign output to prevent deletion of block diagram
- Simulation
 - Counter should increment every system clock
 - We should see the system clock divided by 4
 - We will get rid of this later

```

module clk_gen (
  // global signals
  i_reset_n,
  i_clk,
  // Strobe from 32,768 Hz reference clock
  i_refclk,
  // output strobe signals
  o_1hz_stb, // refclk / 2^15 -> 1Hz
  o_slow_set_stb, // refclk / 2^14 -> 2Hz
  o_fast_set_stb, // refclk / 2^12 -> 8Hz
  o_debounce_stb // refclk / 2^4 -> 4.096KHz
);

input wire i_reset_n;
input wire i_clk;
input wire i_refclk;

output wire o_1hz_stb;
output wire o_slow_set_stb;
output wire o_fast_set_stb;
output wire o_debounce_stb;

wire refclk_stb;

reg [14:0] counter;
always @(posedge i_clk) begin
  counter <= counter + 15'd1;
  if (!i_reset_n) begin
    counter <= 15'd0;
  end
end

assign o_1hz_stb = counter[2];

endmodule

```

Expected Block Diagram

- Generate block diagram
 - `elaborate_json.bat clk_gen src\input\clk_gen.v`
 - This copies the block diagram into your clipboard
- Generate Picture
 - Go to <https://neilturley.dev/netlistsvg/>
 - Paste in code
 - Click "render"

```

C:\WINDOWS\system32\cmd.exe
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>elaborate_json.bat clk_gen src\input\clk_gen.v
    
```


Commands are run from the project directory

This is a demo of [netlistsvg](https://neilturley.dev/netlistsvg/).

Format JSON Select skin: `lib/default.svg` Render


```

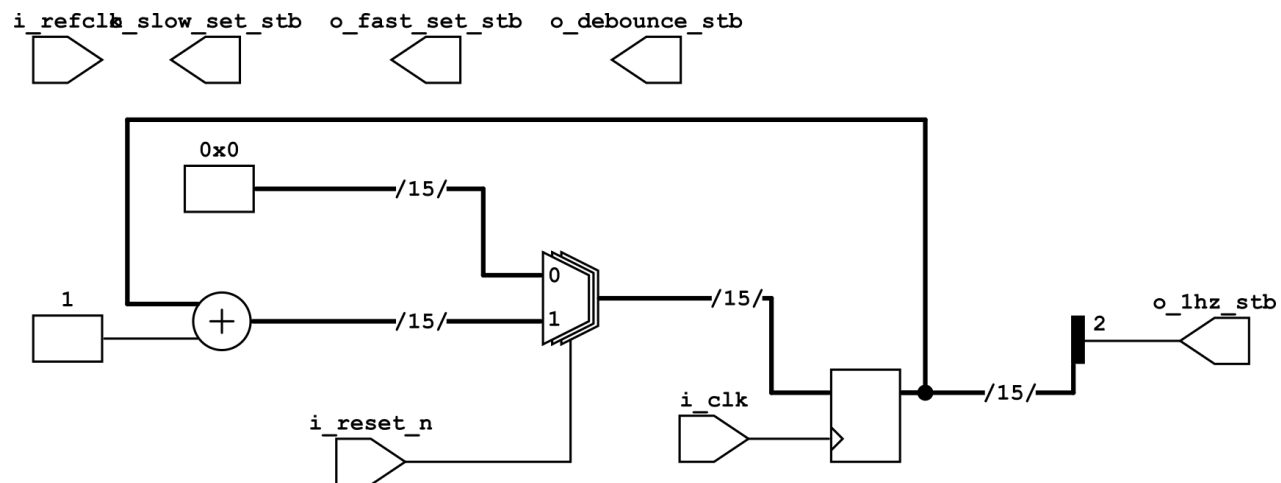{
  "attributes": {
    "src": "src\\input\\clk_gen.v:45.1-50.4"
  },
  "port_directions": {
    "CLK": "input",
    "D": "input",
    "Q": "output"
  },
  "connections": {
    "CLK": [ 3 ],
    "D": [ 38, 39, 40, 41, 42, 43, 44, 45, 46, 47,
48, 49, 50, 51, 52 ],
    "Q": [ 9, 10, 5, 11, 12, 13, 14, 15, 16, 17, 18,
19, 20, 21, 22 ]
  },
  "$procmux$4": {
    
```



Expected Counter Output

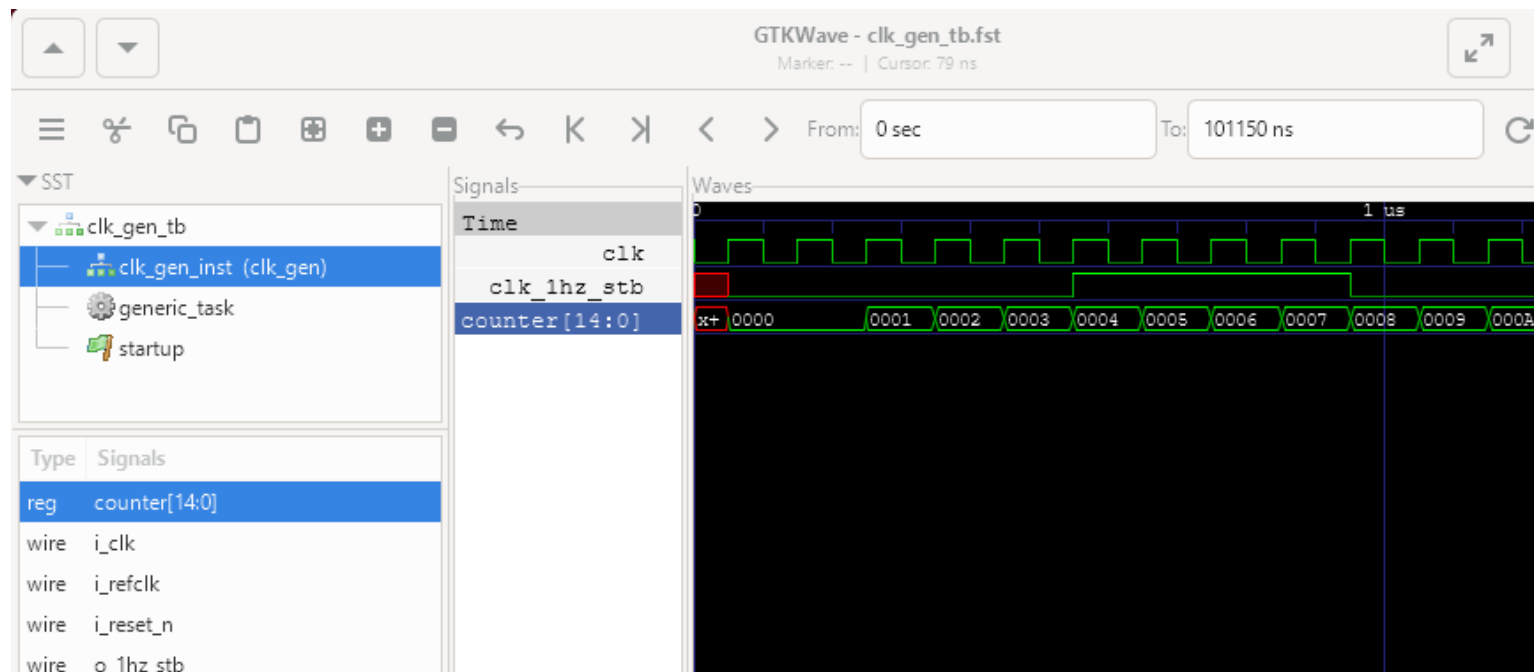- Run Simulator
 - `iverilog -o clk_gen_tb.vvp test\clk_gen_tb.v src\input\clk_gen.v`
 - `vvp clk_gen_tb.vvp -fst`
- Open Waveform Viewer
 - Do this in a different terminal
 - `gtkwave clk_gen_tb.fst`



```

C:\WINDOWS\system32\cmd.exe Run Simulator
[OSS CAD Suite] D:\clock_2024_worksh
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>iverilog -o clk_gen_tb.vvp test\clk_gen_tb.v src\input\clk_gen.v
[OSS CAD Suite] D:\clock_2024_workshop>vvp clk_gen_tb.vvp -fst_
  
```

```

C:\WINDOWS\s Run gtkwave en_tb.fst
[OSS CAD Suite] D:\clock_2024_workshop>gtkwave clk_gen_tb.fst


GTKWave Analyzer v3.4.0 (w)1999-2022 BSI

FSTLOAD | Processing 26 facs.
FSTLOAD | Built 19 signals and 7 aliases.
FSTLOAD | Building facility hierarchy tree.
FSTLOAD | Sorting facility hierarchy tree.
  
```


Commands are run from the project directory

Generating Strobe Signals

 - Output '1' on signal rising edge
- Detect rising edge
 - Hold the previous signal state
 - Compare to current signal state
 - Output '1' when previous state is '0' and current state is '1'
- Reset when **i_reset_n** is low
- Put this into a new module
 - The new module should be in the same file as the counter module



Combinational Logic: Assign statement

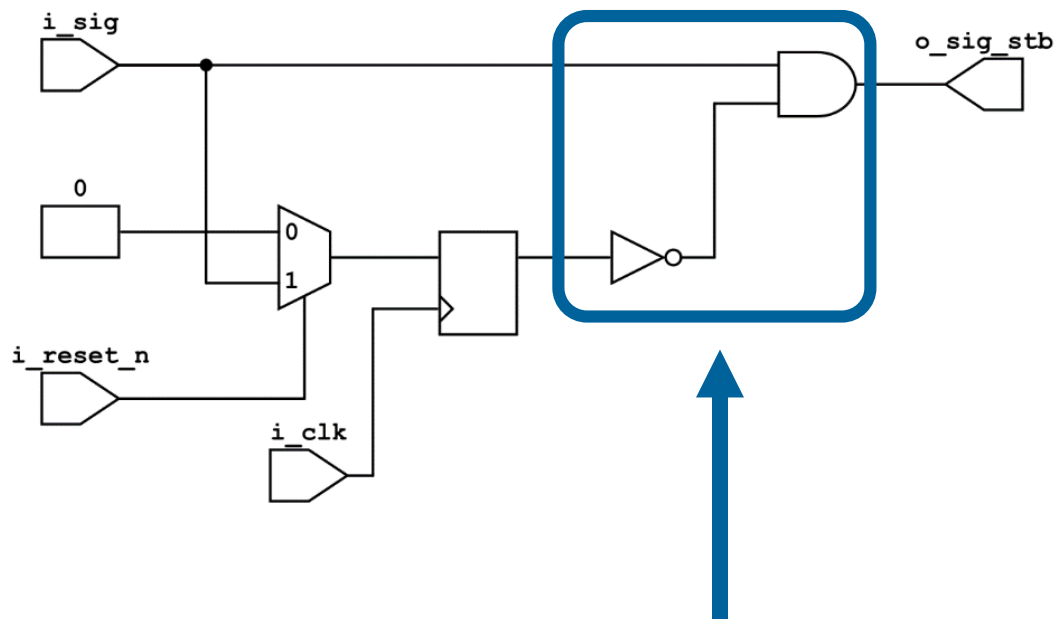


```
assign o_sig_stb = i_sig & ~sig_hold;
```

- In general:
assign wire_name
= signal1 [operation signal2 ...];
- Signals can be either wires or regs
- Can only assign to wires
- Assign statements cannot be in always blocks

Strobe Generator Code

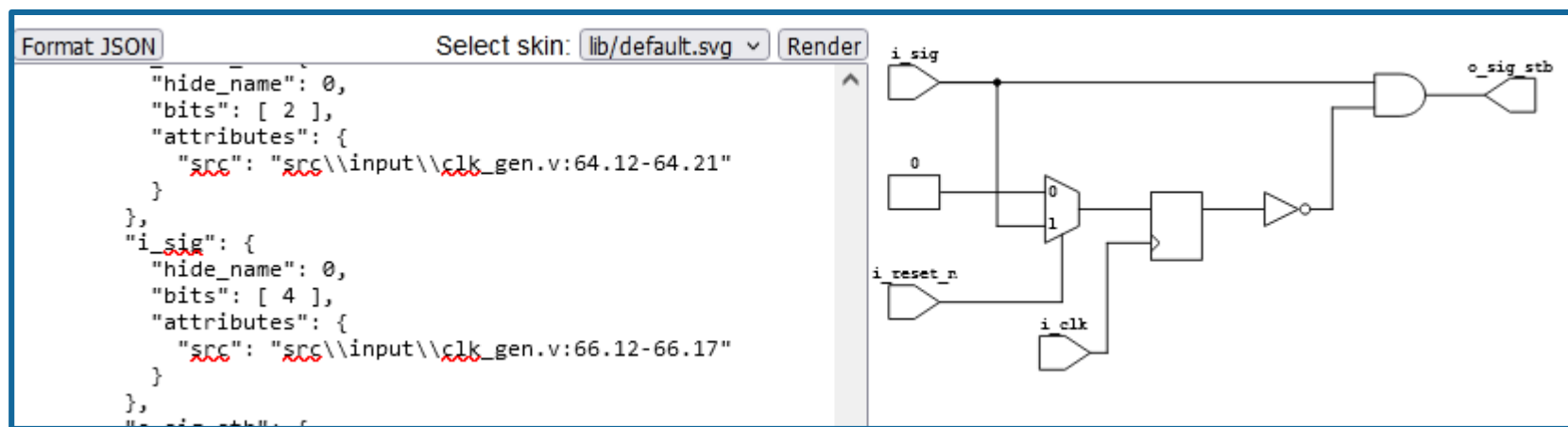- Example Strobe Generator
- Generate Block Diagram
 - `elaborate_json.bat stb_gen src\input\clk_gen.v`
 - Paste into netlistsvg



```

assign o_1hz_stb = counter[2];

endmodule
End of clk_gen

module stb_gen (
    i_reset_n,
    i_clk,

    i_sig,
    o_sig_stb
);


input wire i_reset_n;
input wire i_clk;
input wire i_sig;
output wire o_sig_stb;

reg sig_hold;
always @(posedge i_clk) begin
    sig_hold <= i_sig;
    if (!i_reset_n) begin
        sig_hold <= 1'b0;
    end
end

assign o_sig_stb = i_sig & ~sig_hold;

endmodule
    
```


Fixing the counter

 

- We only want to count up on the rising edge of refclk
- Generate a strobe signal off of refclk (**refclk_stb**)
 - Instantiate a module that we just made
 - Input signal is **refclk**, generates **refclk_stb**
 - Only count up when **refclk_stb** is high
 - This makes our counter work right.
- Generate strobe signals for each output clock.
 - Do the same thing, but take strobe input from counter register

Instantiating Modules

- Back to Modules
- How do we instantiate a module?

```

module_name #(parameter list)
instance_name (
    .port_name1 (connected signal 1),
    .port_name2 (connected signal 2)
);
    
```

I'm not using this. Just FYI

```

// clock strobe generator signals
wire refclk_sync;
wire clk_1hz_stb;
wire clk_slow_set_stb;
wire clk_fast_set_stb;
wire clk_debounce_stb;
    
```

Define Signals

```

clk_gen clk_gen_inst (
    .i_reset_n (reset_n),
    .i_clk (clk),
    .i_refclk (refclk_sync),
    .o_1hz_stb (clk_1hz_stb),
    .o_slow_set_stb (clk_slow_set_stb),
    .o_fast_set_stb (clk_fast_set_stb),
    .o_debounce_stb (clk_debounce_stb)
);
    
```

Instantiate Clock Generation Module

```

// Generate a strobe signal on reference clock rising edge
wire refclk_stb;
stb_gen refclk_stb_inst (
    .i_reset_n (i_reset_n),
    .i_clk (i_clk),
    .i_sig (i_refclk),
    .o_sig_stb (refclk_stb)
);
    
```

Instantiate Strobe Generation Module



Updated Clock Generator

- Add refclk strobe generator
- Only update counter on **refclk** rising edge
 - Check if **refclk_stb** is high before incrementing
- Generate slower strobos
 - Strobe on $\frac{\text{refclk}}{2^{15}}$, $\frac{\text{refclk}}{2^{14}}$, $\frac{\text{refclk}}{2^{12}}$, and $\frac{\text{refclk}}{2^4}$
 - Generates 1Hz, 2Hz, 8Hz, and 4.096KHz strobos

```
// Generate a strobe signal on reference clock rising edge
wire refclk_stb;
stb_gen refclk_stb_inst (
  .i_reset_n (i_reset_n),
  .i_clk     (i_clk),
  .i_sig     (i_refclk),
  .o_sig_stb (refclk_stb)
);
```

refclk

Instantiate Strobe Generation Module

```
reg [14:0] counter;
// TODO Add counter logic
always @(posedge i_clk) begin
  if (refclk_stb) begin
    counter <= counter + 15'd1;
  end
  if (!i_reset_n) begin
    counter <= 15'd0;
  end
end

// generate strobe signals off of the clock divider
// 32,768 / 2^15 -> 1hz
stb_gen stb_gen_1hz (
  .i_reset_n (i_reset_n),
  .i_clk     (i_clk),
  .i_sig     (counter[14]),
  .o_sig_stb (o_1hz_stb)
);

// 32,768 / 2^13 -> 2hz
stb_gen stb_gen_slow_clk (
  .i_reset_n (i_reset_n),
  .i_clk     (i_clk),
  .i_sig     (counter[13]),
  .o_sig_stb (o_slow_set_stb)
);

// 32,768 / 2^11 -> 8hz
stb_gen stb_gen_fast_clk (
  .i_reset_n (i_reset_n),
  .i_clk     (i_clk),
  .i_sig     (counter[11]),
  .o_sig_stb (o_fast_set_stb)
);

// 32,768 / 2^3 -> 4096Hz
stb_gen stb_gen_debounce_clk (
  .i_reset_n (i_reset_n),
  .i_clk     (i_clk),
  .i_sig     (counter[3]),
  .o_sig_stb (o_debounce_stb)
);

endmodule
```

counter

÷ 2¹⁵



÷ 2¹⁴

÷ 2¹²

÷ 2⁴


Clock Generator

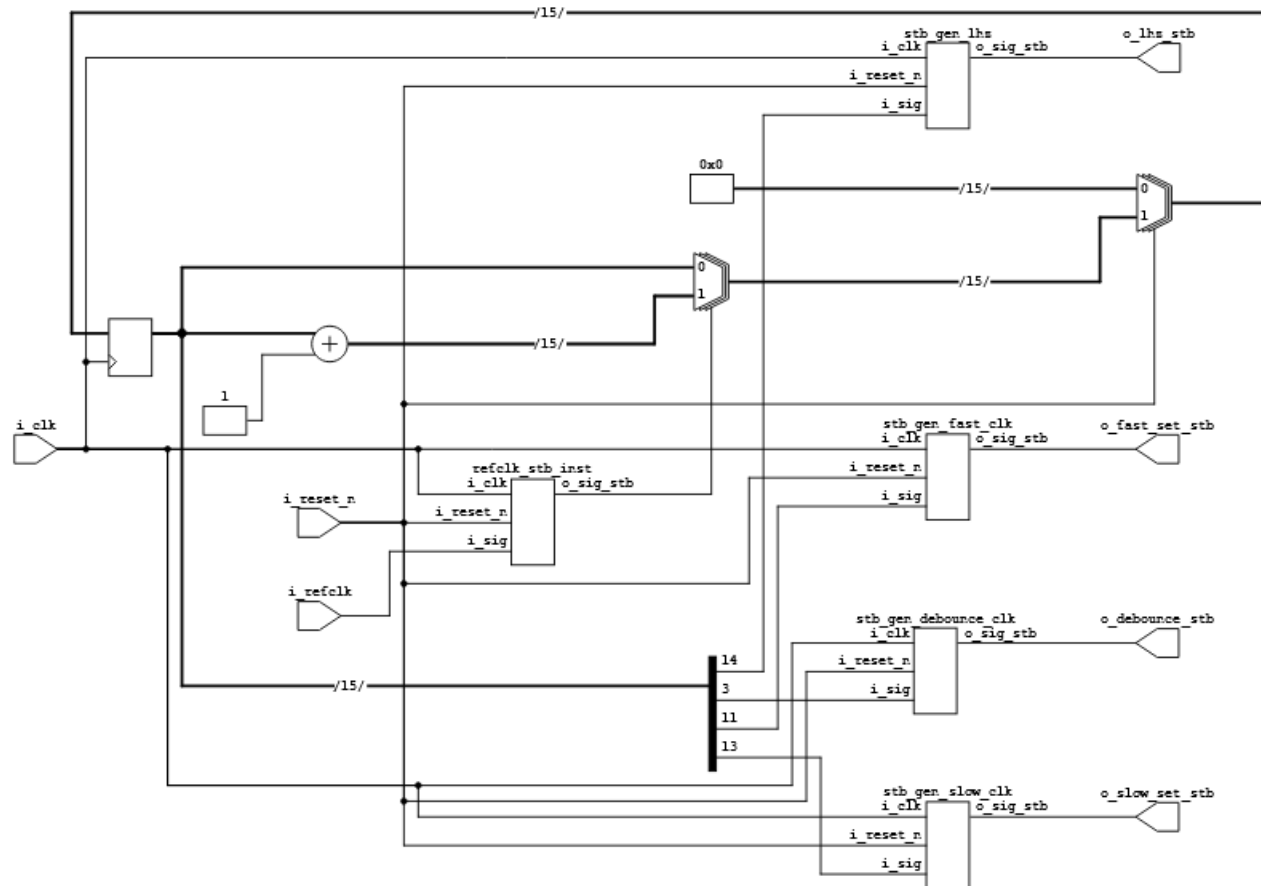 
- Generate Block Diagram
 - `elaborate_json.bat clk_gen src\input\clk_gen.v`
 - Paste into netlistsvg
- Run Simulation
 - `iverilog -o clk_gen_tb.vvp test\clk_gen_tb.v src\input\clk_gen.v`
 - `vvp clk_gen_tb.vvp -fst`
- Refresh Simulator Output



Expected Output

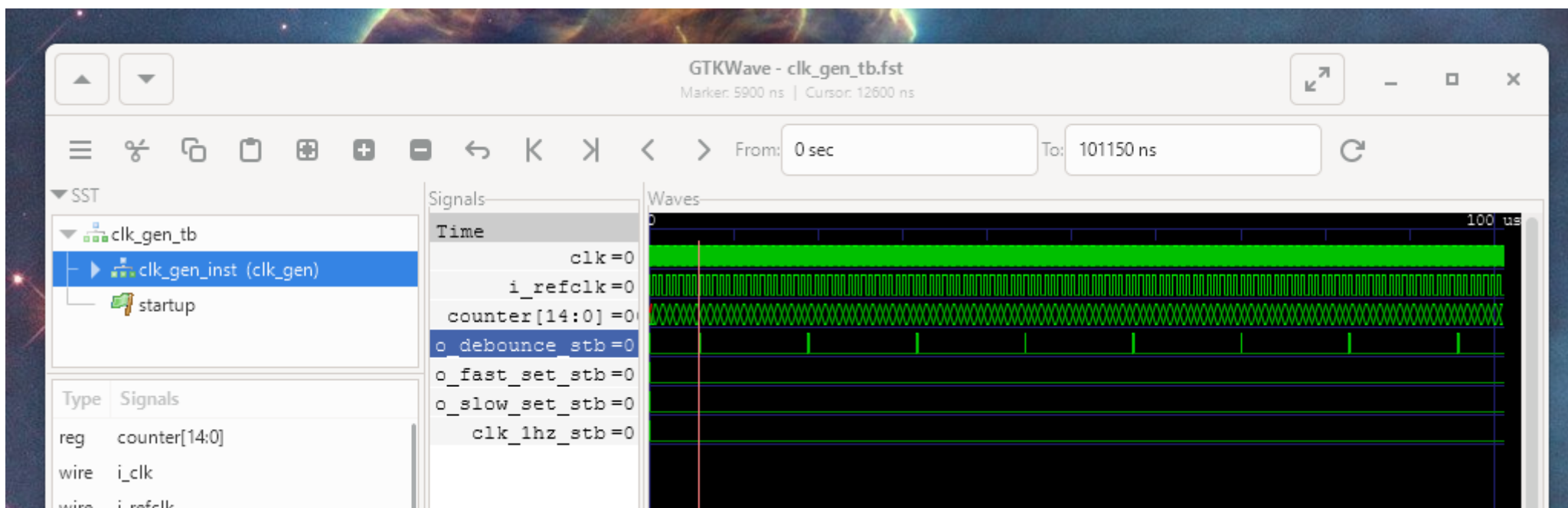- Should see pulses on **o_debounce_stb** signal
- Where are our other pulses?
 - We aren't waiting long enough
 - Take a closer look at testbenches next




 


What have we learned?

- Write basic modules
 - Sequential logic with “always @(posedge i_clk)”
 - Sequential logic with “assign”
 - Generate Strobe signals to trigger events
- View block diagrams
 - Use yosys to elaborate designs
 - View with [netlistsvg](#)
- Run Simulator
 - Use verilator to simulate Verilog module
 - Use gtkwave to view output

Writing Verilog Testbenches

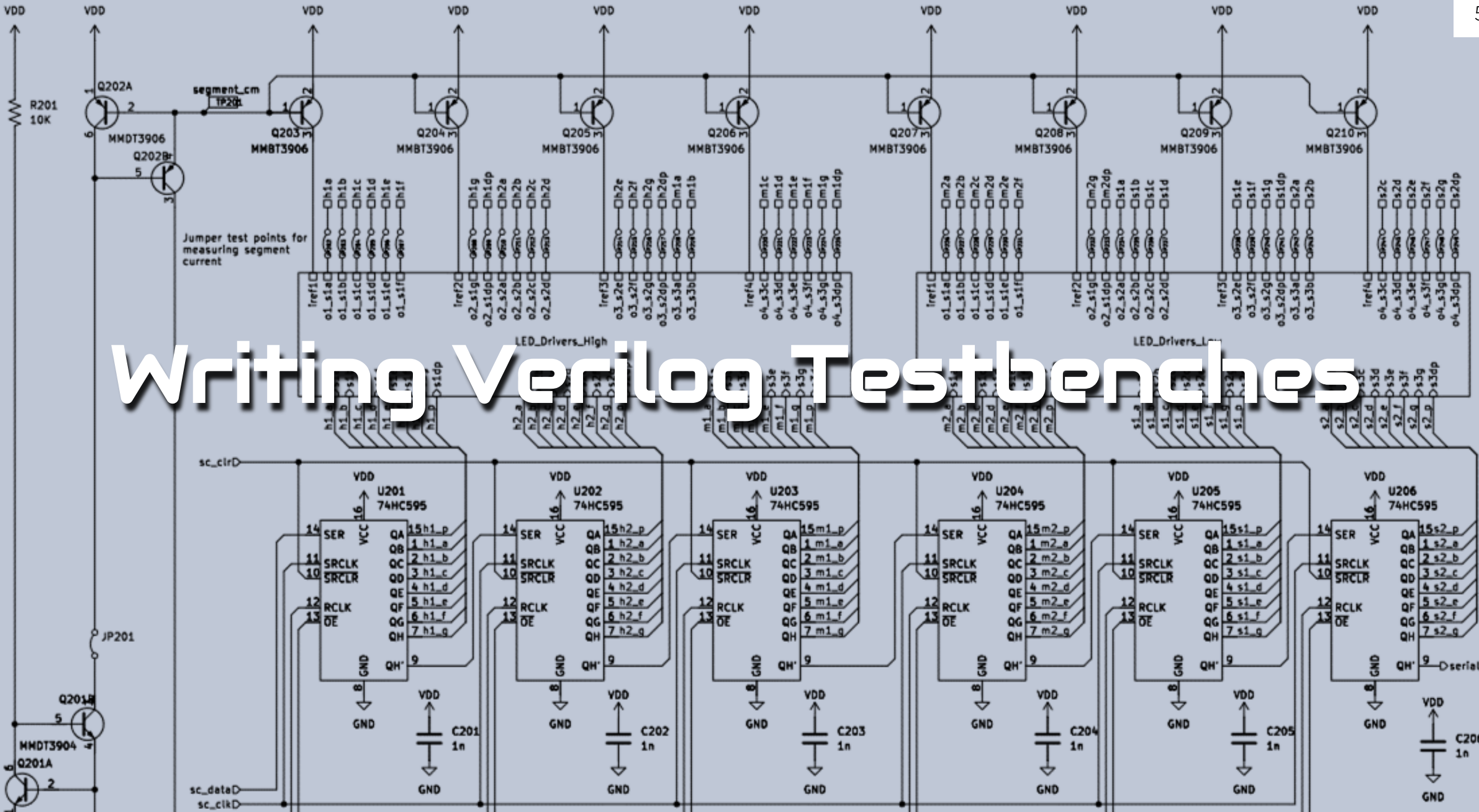

Writing Verilog Testbenches

 

- So far we've used a very basic testbench
 - It just runs the system clock for 1000 cycles
 - No checks on the output are run
- We want to look at writing better testbenches
 - Failure output if module output doesn't match expectations
 - Similar to unit tests from software
- Using Verilog tasks to make life easier
 - More like using a normal programming language

Open clk_gen_tb Testbench

- Open ``test\clk_gen_tb.v``
- Notable things
 - Testbench is a Verilog module
 - Takes no inputs
 - Produces no outputs
 - Less strict rules
 - This doesn't get turned into hardware
 - Use "=" in tasks
- Let's go on a tour
 - Assert definitions
 - Module definition

```

// Assert helpers for ending the simulation early in failure
define assert(signal, value) \
    if (signal != value) begin \
        $display("ASSERTION FAILED in %m:\nEquality"); \
        $display("\t%d (expected) != %d (actual)", value, signal); \
        close(); \
    end

define assert_cond(signal, cond, value) \
    if (!(signal cond value)) begin \
        $display("ASSERTION FAILED in %m:\nCondition:"); \
        $display("\n\texpected: %d\n\tactual: %d", value, signal); \
        close(); \
    end

define assert_timeout(max_count) \
    if (!(timeout_counter < max_count)) begin \
        $display("ASSERTION FAILED in %m\nTimeout:"); \
        $display("\n\tspecified max count: %d\n\tactual count: %d", max_count, \
            timeout_counter); \
        close(); \
    end
    
```

Assert Definitions

```


module clk_gen_tb ();
    // cocoth interface signals

    reg test_done = 0;

    // global parameters
    localparam CLK_PERIOD = 100;
    localparam REFCLK_PERIOD = 203;
    localparam TIMEOUT = 5000;
    
```

Module Definition

Testbench: Startup (1/2)

 


```
33 module clk_gen_tb ();
34     // cocotb interface signals
35     reg test_done = 0;
36
37     // global parameters
38     localparam CLK_PERIOD = 100;
39     localparam REFCLK_PERIOD = 203;
40     localparam TIMEOUT = 5000;
41     localparam STARTUP_DELAY = 5;
42
43     // global testbench signals
44     reg clk = 0;
45     reg reset_n = 0;
46     reg ena = 1;
47     reg refclk = 0;
48
49     reg run_timeout_counter;
50     reg [15:0] timeout_counter = 0;
```

- Local parameters act as constants
- Used throughout testbench to reduce “magic numbers”

- Set initial values on registers
- Puts registers into well defined state at startup

Testbench: Module Initialization

 

```
52 // Output signals from device-under-test (DUT)
53 wire clk_1hz_stb;
54 wire clk_slow_set_stb;
55 wire clk_fast_set_stb;
56 wire debounce_stb;
57
58 // setup top level testbench signals
59 clk_gen clk_gen_inst (
60     // global signals
61     .i_reset_n(reset_n),
62     .i_clk(clk),
63     // Strobe from 32,768 Hz reference clock
64     .i_refclk(refclk),
65     // output strobe signals
66     .o_1hz_stb(clk_1hz_stb), // refclk / 2^15 -> 1Hz
67     .o_slow_set_stb(clk_slow_set_stb), // refclk / 2^14 -> 2Hz
68     .o_fast_set_stb(clk_fast_set_stb), // refclk / 2^12 -> 8Hz
69     .o_debounce_stb(debounce_stb) // refclk / 2^4 -> 4.096KHz
70 );
```

- Define signals generated by device-under-test

- Setup DUT
- We can instantiate more modules for helping out
- Any other modules need added to simulator sources

Testbench: Startup (2/2)

```

72 // setup file dumping things
73 initial begin: startup
74     integer i;
75 // Set the output file to dump to
76     $dumpfile("clk_gen_tb.fst");
77     $dumpvars(0, clk_gen_tb);
78     #STARTUP_DELAY;
79
80     $display("Clock Strobe Generation Testbench");
81     init();
82
83 // TODO: Make testbench fancy
84 // This just runs for 1000 clock cycles then quit
85     for (i = 0; i < 1000; i = i + 1) begin
86         @(posedge clk);
87         // $display("%d", clk_1hz_stb);
88     end
89
90     test_done = 1;
91     // exit the simulator
92     close();
93 end

```

- **initial** block is run on startup
- Name provided so that variables can be used in block.
 - **begin: <block name>**
- **integer i** counter variable definition
 - 32-bit local variable
- **\$dumpfile(<string>)**
 - specify output file name
- **\$dumpvars(0, <modules/variables>)**
 - Save waveform outputs from a module
 - See Verilog Reference 18.1.2
- **\$display(<format>, <list of vals>)**
 - Works like printf
- Call **init()** task
- Run simulation for 1000 clock cycles

Testbench: Default Tasks

```

117 task init();
118     begin
119         $display("Simulation Start");
120         $display("Reset");
121
122         repeat (2) @(posedge clk);
123         reset_n = 1;
124         $display("Run");
125     end
126 endtask

```

```

128 task close();
129     begin
130         $display("Closing");
131         repeat (10) @(posedge clk);
132         $finish;
133     end
134 endtask

```

- In general:


```

task task_name ( input input1, ... );
begin: <block_name>
    // stuff
end
endmodule
            
```

- Reset the system
 - Assert **reset_n** for two clock cycles

- Delay a bit before ending the simulation
- Makes it easier to read waveforms

\$finish closes the simulator

Testbench: Clock Generation

```

136 task reset_timeout_counter();
137 begin
138     @(posedge clk);
139     run_timeout_counter = 1'd0;
140     @(posedge clk);
141     run_timeout_counter = 1'd1;
142 end
143 endtask
144
145 // System Clock
146 localparam CLK_HALF_PERIOD = CLK_PERIOD / 2;
147 always #(CLK_HALF_PERIOD) begin
148     clk <= ~clk;
149 end
150
151 // Reference clock
152 localparam REFCLK_HALF_PERIOD = REFCLK_PERIOD / 2;
153 always #(REFCLK_HALF_PERIOD) begin
154     refclk <= ~refclk;
155 end
156
157 // Timeout Clock
158 always @(posedge clk) begin
159     if (run_timeout_counter) timeout_counter <= timeout_counter + 1'd1;
160     else timeout_counter <= 16'h0;
161 end


```

- Task to clear the timeout counter
 - More to follow later

- Periodically toggle clock registers
 - `always #(<delay_time>)`

- Run the timeout counter
 - `always #(<delay_time>)`

Testbench: User Task

 

```
98 task generic_task(  
99     input integer timeout  
100 );  
101 begin : my_generic_task  
102     $display("Timeout: %d", timeout);  
103  
104     // reset our watchdog timer  
105     reset_timeout_counter();  
106  
107     while ( /* some condition */ timeout_counter < timeout) begin  
108         // TODO: Implement the generic task we want to accomplish  
109         @(posedge clk);  
110     end  
111  
112     // make sure we didn't run out the watchdog timer  
113     `assert_timeout(timeout);  
114 end  
115 endtask
```

• We will edit this task for our testbench

• Input value to task

- We use this to set the maximum count for the timeout counter

• Reset the timeout counter so that we can check its value from a known state

• Loop until a condition is met
• Exit the loop if we are over the timeout
• One clock cycle per loop iteration

• Assert that we passed the condition and didn't timeout

Edit the testbench

- Call the user task
 - Remove the for loop
- Run the simulator
 - Same command as before
 - Should see timeout failure

```

C:\WINDOWS\system32\cmd.exe
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>
[OSS CAD Suite] D:\clock_2024_workshop>iverilog -o clk_gen_tb.vvp test\clk_gen_tb.v src\input\clk_gen.reference

[OSS CAD Suite] D:\clock_2024_workshop>vvp clk_gen_tb.vvp -fst
FST info: dumpfile clk_gen_tb.fst opened for output.
Clock Strobe Generation Testbench
Simulation Start
Reset
Run
Timeout:          5000
ASSERTION FAILED in clk_gen_tb.generic_task
Timeout:
    specified max count:      5000
    actual count: 5000
Closing
test\clk_gen_tb.v:127: $finish called at 501450 (1ns)
[OSS CAD Suite] D:\clock_2024_workshop>_

```

```

72 // setup file dumping things
73 initial begin: startup
74     integer i;
75     // Set the output file to dump to
76     $dumpfile("clk_gen_tb.fst");
77     $dumpvars(0, clk_gen_tb);
78     #STARTUP_DELAY;
79
80     $display("Clock Strobe Generation Testbench");
81     init();
82
83     generic_task(TIMEOUT);
84
85     test_done = 1;
86     // exit the simulator
87     close();
88 end

```


Make our test snazzy

- Check that we have the correct number of pulses
 - Add a counters for each pulse generator
- Update task to check correct operation
 - Assert statements to generate failure logs
 - “===” checks against invalid and tristate conditions

```
72 reg [15:0] slow_stb_count = 0;
73 reg [15:0] fast_stb_count = 0;
74 reg [15:0] debounce_stb_count = 0;
75 always @(posedge clk) begin
76     if (clk_slow_set_stb) begin
77         slow_stb_count <= slow_stb_count + 1;
78     end
79
80     if (clk_fast_set_stb) begin
81         fast_stb_count <= fast_stb_count + 1;
82     end
83
84     if (debounce_stb) begin
85         debounce_stb_count <= debounce_stb_count + 1;
86     end
87 end
```

```
110 task generic_task(
111     input integer timeout
112 );
113 begin : my_generic_task
114     $display("Timeout: %d", timeout);
115
116     // reset our watchdog timer
117     reset_timeout_counter();
118
119     // wait for the first 1hz strobe signal
120     $display("Wait for 1hz Strobe Signal");
121     while ( !clk_1hz_stb && timeout_counter < timeout) begin
122         @(posedge clk);
123     end
124     // make sure we didn't run out the watchdog timer
125     `assert_timeout(timeout);
126
127     // reset our watchdog timer
128     reset_timeout_counter();
129     // clear our counter registers
130     slow_stb_count = 0;
131     fast_stb_count = 0;
132     debounce_stb_count = 0;
133
134     $display("Wait for 2nd 1hz Strobe Signal");
135     while ( !clk_1hz_stb && timeout_counter < timeout) begin
136         @(posedge clk);
137     end
138
139     // make sure we didn't run out the watchdog timer
140     `assert_timeout(timeout);
141
142     // assert that we get the correct number of counts
143     // in our counting registers
144     `assert_cond(slow_stb_count, ===, 2);
145     `assert_cond(fast_stb_count, ===, 8);
146     `assert_cond(debounce_stb_count, >=, 1000);
147
148 end
149 endtask
```

To the Simulator!

- Run simulator
- Expected Simulator log
- Should see our pulses in gtkwave


```

C:\WINDOWS\system32\cmd.exe
Closing
test\clk_gen_tb.v:166: $finish called at 3001450 (1ns)

[OSS CAD Suite] D:\clock_2024_workshop>iverilog -o clk_gen_tb.vvp test\clk_gen_tb.v src\input\clk_gen.reference.v

[OSS CAD Suite] D:\clock_2024_workshop>vvp clk_gen_tb.vvp -fst
FST info: dumpfile clk_gen_tb.fst opened for output.
Clock Strobe Generation Testbench
Simulation Start
Reset
Run
Timeout:      300000
Wait for 1hz Strobe Signal
Wait for 2nd 1hz Strobe Signal
Closing
test\clk_gen_tb.v:166: $finish called at 9929950 (1ns)

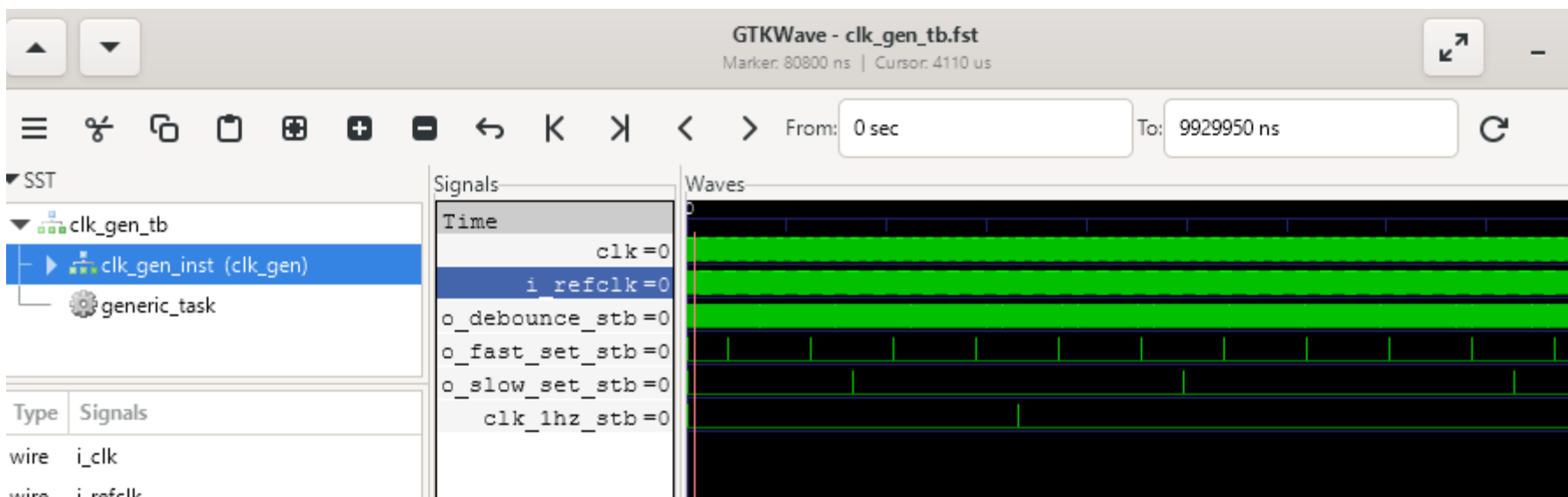[OSS CAD Suite] D:\clock_2024_workshop>_
  
```



Write the Clock Register Module

- Store Hours, Minutes, Seconds
- Normal Operation
 - Count up when 1Hz strobe signal is high
 - Overflow Seconds and count up minutes
 - Overflow Minutes and count up hours
- Time Set
 - When **i_set_hours** is asserted
 - Switch to using the **i_set_stb** signal
 - Increment hours when **i_set_stb** is high
 - When **i_set_minutes** is asserted
 - Switch to using the **i_set_stb** signal
 - Increment hours when **i_set_stb** is high
 - When both are asserted
 - Clear the seconds register

How to draw an Owl.

"A fun and creative guide for beginners"


 


Fig 1. Draw two circles

 

Fig 2. Draw the rest of the damn Owl

We need to update the project



70

- Push changes to Github
- The Github actions will run
 - We (hopefully) see cool output

Update README · sellicott/selli · X

https://github.com/sellicott/sellicott_tt_7seg_clock_2024/actions/runs/11658855406

Code Issues Pull requests **Actions** Projects Security Insights Settings

test

Update README #46 Re-run all jobs

Summary

Jobs

- test

Run details

- Usage
- Workflow file

| Triggered via | Status | Total duration | Artifacts |
|---------------------------------|---------|----------------|-----------|
| sellicott pushed → 7bd8ab5 main | Success | 5m 42s | 1 |

test.yaml


on: push

- test 5m 32s

What have we learned?

- Write basic modules
 - Sequential logic with “always @(posedge i_clk)”
 - Sequential logic with “assign”
- View block diagrams
 - Use yosys to elaborate designs
 - View with [netlistsvg](#)
- Write testbench to simulate modules
 - Simulate with Icarus Verilog
 - View results with gtkwave

Things to look at

 


72

- Detailed Verilog Tutorials

- [NandLand](#)
- [ChipVerify](#)
- [ZipCPU](#)

- Tiny Tapeout Demoscene

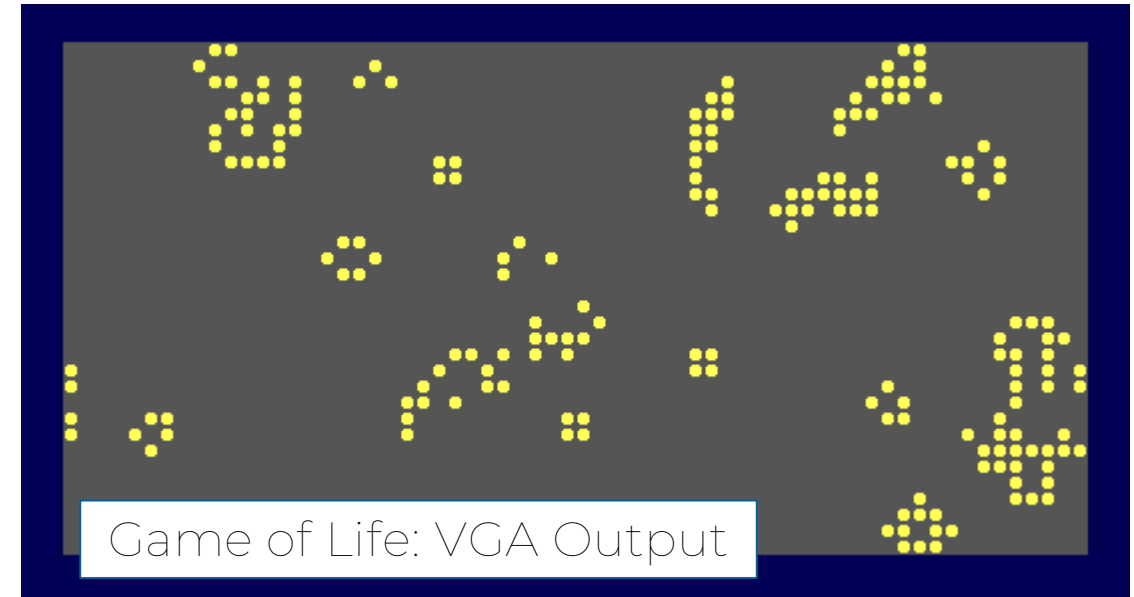- <https://tinytapeout.com/competitions/demoscene/>
- <https://vga-playground.com/>



Where To Get Help

Here!



- Tiny Tapeout Discord
 - Lots of people with deeper knowledge than me
 - I'm there too (@sellicott)


- Learning Resources
 - https://tinytapeout.com/digital_design/
 - <https://tinytapeout.com/hdl/>
 - <https://r2.ieee.org/columbus-ssccas/resources/>

- Questions about this workshop
 - Chapter: columbus.sscs.cas@gmail.com




Tiny Tapeout Discord
<https://discord.gg/BspcX9SB2h>

Acknowledgements

 

Matt Venn

 - [Original workshop slides](#)
- Advice on running a workshop




Everyone who worked on Tiny Tapeout!



<https://tinytapeout.com/credits/>

Extra Slide

 

This page unintentionally left blank